

17318

21718

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.

Marks

1. (A) Attempt any SIX of the following : 12

- (a) Define form factor for a sine wave. State its value.
- (b) Define bandwidth of a series resonant circuit and give the expression for the same.
- (c) State two advantages of three phase system over single phase system.
- (d) State Fleming's Right hand rule.
- (e) State Faraday's laws of electromagnetic induction.
- (f) Define slip and slip speed.
- (g) State any two speed control methods for three phase induction motor.
- (h) State the necessity of earthing.

(B) Attempt any TWO of the following : 8

- (a) Draw the waveforms and phasor diagrams to show the relationship between V & I in pure inductive and pure capacitive circuits.
- (b) Draw a neat labelled circuit diagram of three phase delta connected system and write relationship between
 - (i) Line voltage and phase voltage
 - (ii) Line current and phase current.

[1 of 4]

P.T.O.

- (c) Compare squirrel cage & slip ring induction motor based on
- (i) Rotor construction
 - (ii) Starting torque
 - (iii) Efficiency
 - (iv) Application

2. Attempt any FOUR of the following :

16

- (a) Give the definition and expression for the following terms :
- (i) Inductive Reactance
 - (ii) Capacitive Reactance
 - (iii) Impedance
 - (iv) Power Factor
- (b) Explain the phenomenon of resonance in RLC series circuit.
- (c) Draw the circuit diagram, waveforms, equations for V & I and phasor diagram for an R-L series circuit.
- (d) State different types of power in AC circuits. Write its expression and unit.
- (e) State and explain the principle of 3 ϕ emf generation. Draw its waveform.
- (f) Compare autotransformer & two winding transformer. (any 4)

3. Attempt any FOUR of the following :

16

- (a) Compare dc supply with ac supply.
- (b) Define leading and lagging ac quantities. Draw waveform representation and equations representing the same.
- (c) A choke coil is connected across 230 V, 50 Hz supply. The power consumed by the coil is 960 W and current I_{rms} is 8A. Calculate the circuit constants R & L.
- (d) Compare magnetic circuits with electric circuits.
- (e) Explain : (i) Statically induced emf.
(ii) Dynamically induced emf.
- (f) Give constructional features of isolating transformer. State its working principle and applications. (any 2)

4. Attempt any FOUR of the following :**16**

- (a) A coil of resistance 10Ω and 0.1 H is connected in series with a capacitance of $150 \mu\text{F}$ across 230 V , 50 Hz ac supply. Calculate impedance, current, power factor and power consumed by the circuit.
- (b) State the emf equation of a single phase transformer. Define
 - (i) Current Ratio
 - (ii) Transformation Ratio
 - (iii) Voltage Ratio
- (c) Draw and explain torque speed characteristics of 3 phase induction motor.
- (d) Explain the construction and working principle of 3 phase induction motor with a neat diagram.
- (e) Draw schematic representation and explain the principle of working of split phase single phase induction motor.
- (f) Explain the working principle of AC servo motor and state any two applications.

5. Attempt any FOUR of the following :**16**

- (a) An alternating current is given by $i = 10 \sin 628 t$. Calculate
 - (i) Average value
 - (ii) RMS value
 - (iii) Frequency
 - (iv) Time period
- (b) If a 3ϕ 400 V , 50 HZ supply is connected to a balanced 3ϕ star connected load of impedance $(3 + i6) \Omega$ per phase,
Calculate : (i) Phase Current
(ii) Power Factor
(iii) Total Active Power
(iv) Phase Voltage
- (c) A 25 kVA , single phase transformer has 250 turns on the primary and 40 turns on the secondary winding. The primary is connected to 1500 V , 50 Hz mains.
Calculate : (i) Primary and secondary currents on full load.
(ii) Secondary emf.
(iii) Maximum flux on the core.

P.T.O.

- (d) State the necessity of starter in case of three phase induction motor and explain.
- (e) Explain any one method of speed control of single phase induction motor.
- (f) Give any two applications for each,
 - (i) Universal Motor
 - (ii) Stepper Motor
 - (iii) Servo Motor
 - (iv) Split Phase Induction Motor.

6. Attempt any FOUR of the following :

16

- (a) Three impedances each of 3Ω resistance and 5Ω reactance in series are connected in delta across 50 Hz, 440 V line voltage. Find,
 - (i) Impedance
 - (ii) Phase current
 - (iii) Power factor
 - (iv) Total power
 - (b) A 50 kVA, $1 - \phi$ transformer has a full load on loss of 4 kW and iron loss of 2 kW. Find the efficiency of the transformer at half and full load with a power factor of 1.
 - (c) A 20 kVA, 3300/240 V, 50 Hz, $1 - \phi$ transformer has 80 turns on secondary winding. Calculate number of primary turns, full load primary and secondary currents and maximum value of flux in the core.
 - (d) Draw the schematic representation and state the working principle of servo motor.
 - (e) Explain the principle of operation and reversal of rotation of universal motors.
 - (f) State the use of megger. Draw its front panel diagram and different control terminals.
-