

# 17323

11920

3 Hours / 100 Marks

Seat No.


--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.  
(2) Answer each next main Question on a new page.  
(3) Figures to the right indicate full marks.  
(4) Assume suitable data, if necessary.  
(5) Use of Non-programmable Electronic Pocket Calculator is permissible.  
(6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

1. **Attempt any TEN of the following:** **20**

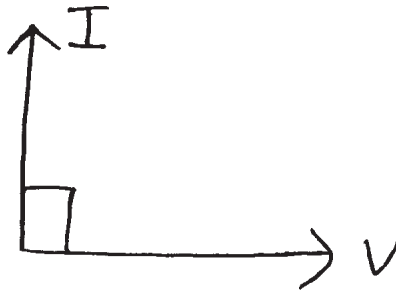- a) Identify/state nature of the circuit of Figure No:1




Identify / State nature of circuit.

**Fig. No. 1**

- b) Define : Frequency and Cycle for AC quantities.  
c) Define : Apparent and Reactive power.  
d) Define : Power factor and Quality factor in RC circuit.  
e) Write equations of resonant frequency and quality factor in terms of circuit components for a parallel circuit.  
f) Define Admittance and Conductance related to parallel circuit.

P.T.O.

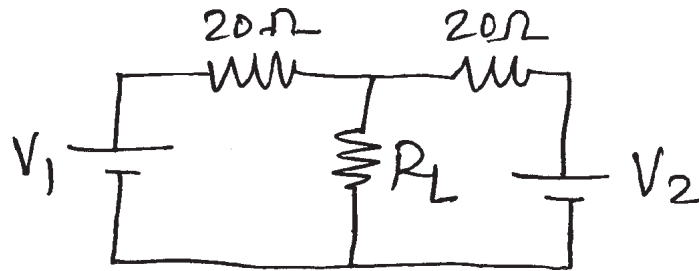- g) State any two advantages of polyphase circuit over single phase circuit.
- h) Draw types of three phase connection.
- i) State the formula for delta to star transformation.
- j) Find the  $R_{TH}$  from Figure No:2



Calculate  $R_{TH}$ .

**Fig. No. 2**

- k) State Norton's theorem for AC circuit.
- l) State meaning of  $t=0^-$  and  $t=0^+$ .

**2. Attempt any FOUR of the following:**

**16**

- a) Instantaneous expression for voltage and current are given by:

$$V = 141.4 \sin 314t$$

$$i = 28.28 \sin (314t + \pi/3)$$

Determine :-

- (i) RMS value of voltage and current
  - (ii) Average value of voltage
  - (iii) Frequency
  - (iv) Power consumed.
- b) For a single loop AC generator :
- (i) Draw a neat sketch
  - (ii) Identify components used
  - (iii) Write equation of generated emf
  - (iv) Draw waveform of the output voltage.

- c) A series circuit has lagging power factor. Draw circuit, waveform and phasor diagrams.
- d) State the values of power factor during resonance condition for RLC series ckt. Also state the importance of power factor.
- e) A coil having a resistance of  $20\Omega$  and inductive reactance of  $47.1\Omega$  is connected in series with a capacitor of reactance  $31.8\Omega$  across an AC supply of 230v.

Determine :


- (i) Current drawn from the supply
  - (ii) Power factor
  - (iii) Active and reactive components of current
  - (iv) Voltage across the coil.
- f) An inductive coil  $(10+j40)\Omega$  impedance is connected in series with a capacitor of  $100\mu\text{F}$  across 230v, 50Hz, 1 ph supply,  
Find : (i) Current through ckt  
(ii) Power factor  
(iii) Power dissipated in ckt  
(iv) Draw phasor diagram.

**3. Attempt any FOUR of the following:**

**16**

- a) Compare series and parallel AC circuit.
- b) Derive the expression for resonant frequency for the series combination of RL in parallel C
- c) An inductor of 0.5H inductance and  $90\Omega$  resistance is connected in parallel with a  $20\mu\text{F}$  capacitor. This circuit supplied by 1 ph, 230v, 50Hz AC supply. Find:
  - (i) The total current
  - (ii) P.F of parallel circuit
  - (iii) Power taken from source
  - (iv) Draw the vector dia.

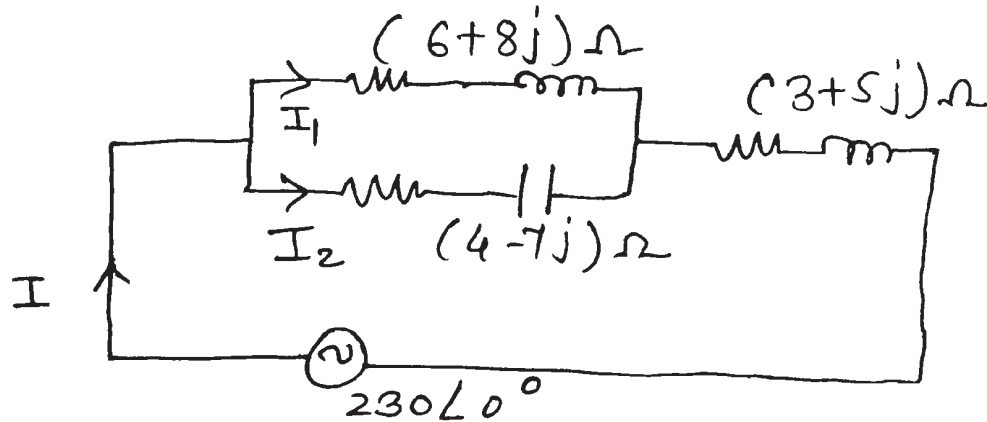- d) Find  $I$ ,  $I_1$ ,  $I_2$  and power factor of ckt in Figure No:3



Calculate  $I$ ,  $I_1$ ,  $I_2$ .

**Fig. No. 3**

- e) Define crest factor and form factor. State value of each for a pure sine wave.
- f) A resistance of  $100\Omega$  and  $50\mu\text{F}$  capacitor are connected in series across  $230\text{V}$ ,  $50\text{Hz}$  supply.  
Find :


- (i) Impedance
- (ii) Current flowing
- (iii) Voltage across R and C
- (iv) PF and power

**4. Attempt any FOUR of the following:**

**16**

- a) Compare balanced and unbalanced three phase load.
- b) A balanced  $\gamma$  connected load with phase impedance of  $14 \angle 45^\circ \Omega$  is connected to a 3ph, 4 wire supply. Having phase vtg of  $231\text{V}$  at  $50\text{Hz}$ . Determine:
  - (i) Line current
  - (ii) Current in neutral wire
  - (iii) Power drawn

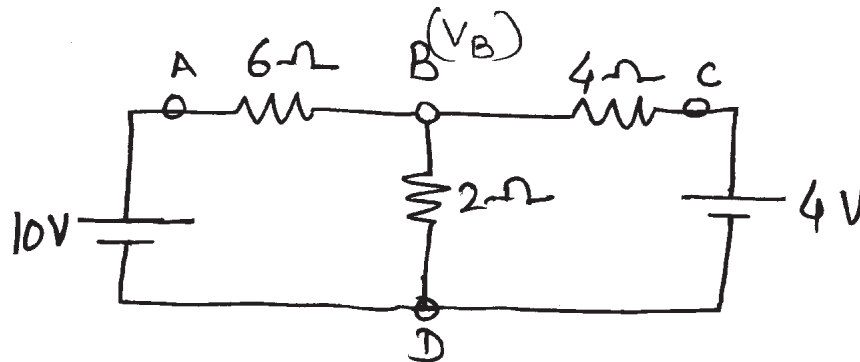
- (iv) Power factor.
- c) A 3ph Y connected load having  $R=15\Omega$ ,  $L=0.04\text{H}$  and  $C=50\mu\text{F}$  in each phase. It is supplied by 440v, 3ph, 50Hz AC. Find :
- 2pH
  - Line current
  - Power factor
  - Power consumed.
- d) Derive the relation for star to delta transformation.
- e) Calculate the node voltage  $V_B$  using the nodal analysis. Refer Figure No:4.



Find  $V_B$  By using (Nodal analysis).

**Fig. No. 4**

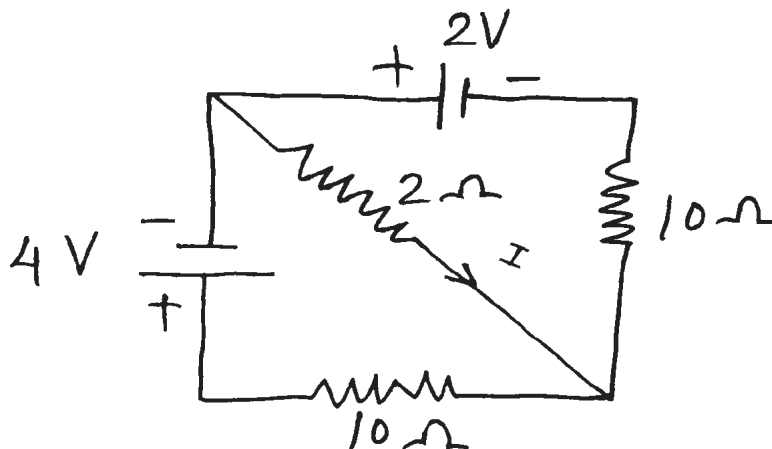- f) Find current  $I$  through  $2\Omega$  using mesh analysis. Refer figure No:5.




Find current  $I$  (By using Mesh analysis).

P.T.O.

**Fig. No. 5**

5. Attempt on TWO of the following:

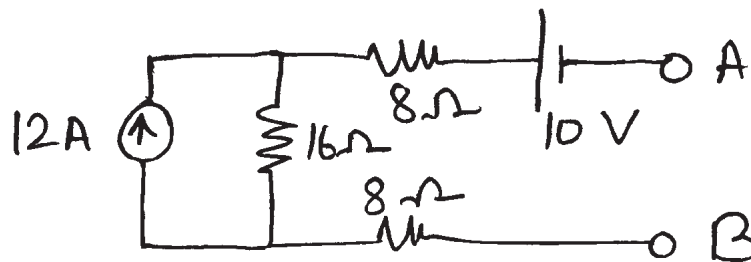- a) With the help of necessary phasor diagram derive the relationship between line and phase current in balanced Y connected load, Connected to 3ph AC supply.
- b) (i) State Thevenins theorem and write its procedural steps to find current in a branch (Assume any simple ckt).  
(ii) Develop Thevenins equivalent across A and B in the network shown in Figure No:6.



Find Thevenin's equivalent circuit.

Fig. No. 6

- c) State the maximum power transfer theorem. In following network shown in Figure No:7, Find the value of  $R_L$  so that maximum power will transfer through it and also calculate this power.




Calculate  $R_L$  (By using Max power transfer theorem).

Fig. No. 7

6. Attempt any **FOUR** of the following:

16

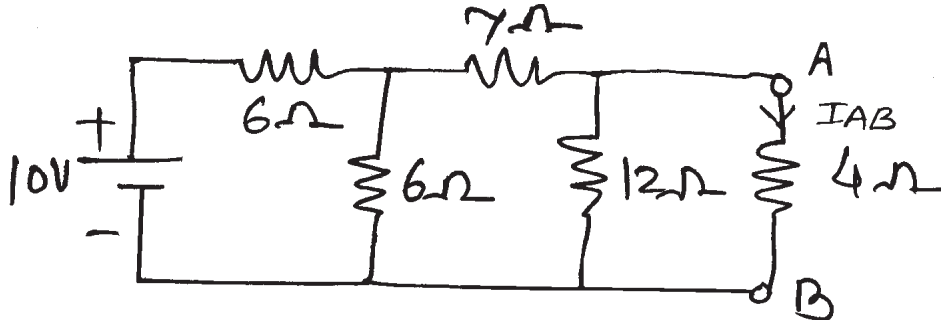
- a) Find current  $I_{AB}$  flowing through  $4\Omega$  resistance using Norton's theorem as shown in FigureNo. 8.



Calculate  $I_{AB}$  (By using Norton's theorem).

Fig. No. 8

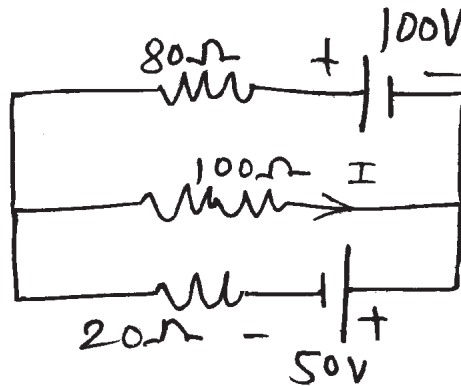
- b) Apply superposition theorem shown in FigureNo. 9 for determining the current  $I$  in  $100\Omega$  resistance.



Calculate  $I$  (By using Superposition theorem).

Fig. No. 9

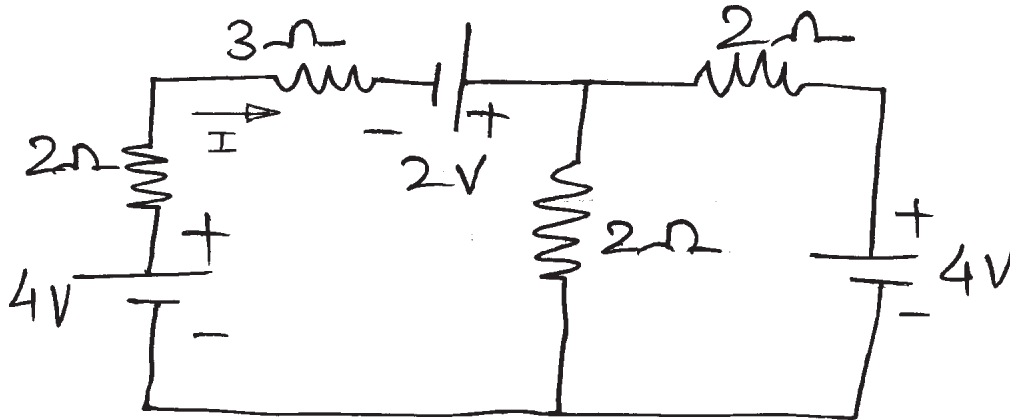- c) Using Node voltage method, find the current  $I$  in the  $3\Omega$  resistance in Figure No:10.



Calculate  $I$  (By using Node voltage method).

**Fig. No. 10**

- d) Current drawn by a 3ph Y connected load of 10A, 0.87 PF lagging when connected across 3ph, 440v AC supply. Find active, reactive and apparent power.
- e) Explain the concept of initial condition switching circuit for the R, L and C.
- f) Define RMS value and average value of AC quantities. State the RMV value and average value in terms of maximum value of sinusoidal waveform.