

17333

11920

3 Hours / 100 Marks

Seat No.

| | | | | | | | | |
|--|--|--|--|--|--|--|--|--|
| | | | | | | | | |
|--|--|--|--|--|--|--|--|--|

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each Section on same / separate answer sheet.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. (A) Attempt any SIX of the following :

12

- (a) Compare analog system with digital system. (any 4 points)
- (b) Perform the following multiplication in binary number system :
 $(15)_{10} \times (8)_{10}$
- (c) Define following characteristics of IC's
 - (i) Propagation delay
 - (ii) Noise immunity
- (d) Draw logic symbol and truth table of two i/p Ex-NOR gate.
- (e) Draw block diagram of 4 : 1 Mux and give it's truth table.
- (f) How many flip-flop are required to construct following modulus counter
 - (i) 56 (ii) 83 (iii) 99 (iv) 10
- (g) List any four applications of A/D converter.
- (h) Write any four Boolean laws used to reduce Boolean Expression.

[1 of 4]

P.T.O.

(B) Attempt any TWO of the following :**8**

- (a) Define the following terms with reference to logic families :
- (i) Threshold voltage
 - (ii) Power dissipation
 - (iii) Operating speed
 - (iv) Logic Voltage level
- (b) State and prove De Morgan's theorems
- (c) Add $(83)_{10}$ and $(34)_{10}$ in BCD.

2. Attempt any FOUR of the following :**16**

- (a) Convert $(2003.31)_{10}$ to hex equivalent.
- (b) Implement the following expression by minimizing the variable using Universal gate

$$Y = A\bar{B} + AB + \bar{A}BC + ABC$$

- (c) Simplify using K map and Realize reduced expression using basic gates
- $$f(A, B, C, D) = \Sigma m(1, 3, 4, 5, 7, 9, 11, 13, 15)$$
- (d) Draw master slave – JK flip-flop using NAND gates and explain its working.
- (e) Draw symbol of D flip-flop and write down it's truth table
- (f) Convert following equation to standard SOP form

$$Y = (A + B\bar{C})(B + AC)$$

3. Attempt any FOUR of the following :**16**

- (a) Design half adder circuit using NOR gates only.
- (b) Describe edge triggered flip-flop with waveforms.
- (c) State any four applications of DAC.

- (d) Draw logic diagram of 1 : 8 demultiplexer. Write its truth table.
- (e) What is race around condition and how it can be avoided ? Explain.
- (f) Design 1 bit comparator using K-map & draw it's logic diagram.

4. Attempt any FOUR of the following :

16


- (a) Draw the logical diagram of MOD 11 counter and describe it's operation with truth table.
- (b) Compare R-2R and Weighted Register DAC.
- (c) Differentiate between Asynchronous and Synchronous counter.
- (d) Classify memories. Give function of each type.
- (e) Compare combinational logic system and sequential logic system.
- (f) Simplify following equation using boolean algebra and draw its circuit diagram :

$$Z = \overline{(X \cdot \overline{W} + \overline{Y} \cdot Z)}(X \cdot W + \overline{Y}Z)$$

5. Attempt any FOUR of the following :

16

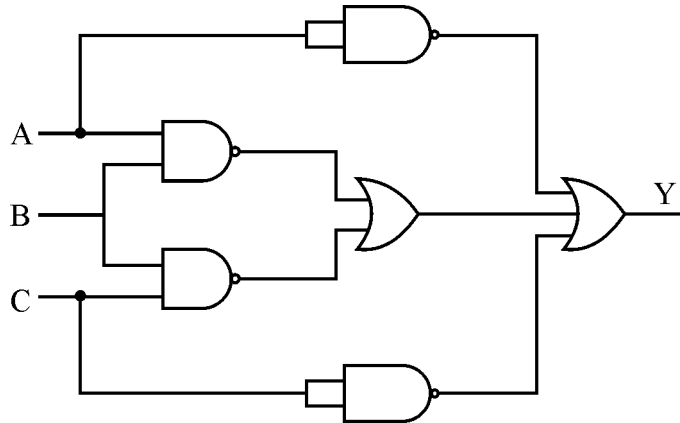- (a) For the logic circuit shown in figure below, what will be the expression for output Y ? Identify the basic gates & universal gates used in ckt.



- (b) Draw and explain SISO with truth table and timing diagram.
- (c) Reduce the following expression using K-map & Implement it using NAND gates

$$Y = \pi M(1, 3, 5, 7, 8, 10, 14)$$


P.T.O.

- (d) Draw & explain block diagram of BCD to seven segment decoder / driver using IC 7447 with it's truth table.
- (e) Draw D flip-flop using
- SR flip-flop
 - Jk flip-flop
- (f) Convert $(6AC)_{16} = (?)_{10} = (?)_2$

6. Attempt any TWO of the following :

16

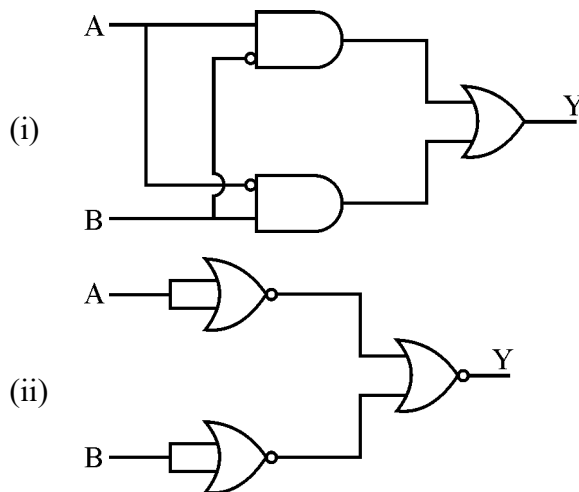- (a) Find the boolean expression for logic circuit given below.



- (b) Convert following expression into standard SOP form.

(i) $\bar{A} + B\bar{C}\bar{D}$

(ii) $A\bar{B}C + B\bar{D}$

- (c) Draw the circuit diagram of 3 bit R-2R ladder DAC. Obtain it's output voltage expression.
-