

# 17415

**16172**

**3 Hours / 100 Marks**

Seat No.

--	--	--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

- 1. Attempt any TEN of the following: **20****
- a) State Fleming's Right Hand Rule.
  - b) Give the two functions of yoke in DC machine.
  - c) State the principle of operation of a dc motor.
  - d) Write the voltage and power equation of a dc motor.
  - e) How will you change the direction of rotation of a d.c. motor?
  - f) A dc motor operating on a supply voltage of 200V dc has armature resistance of  $0.5\Omega$ . If its armature current is 25A, Calculate the back emf.

P.T.O.

- g) Define:
- (i) Transformation Ratio
  - (ii) Turns
- Ratio related to 1- $\phi$  Transformer.
- h) State working principle of a transformer.
- i) Name the two components of no load current  $I_0$  of 1- $\phi$  Transformer and also write down their formulae.
- j) State the condition for maximum efficiency for single phase transformer.
- k) State any two advantage of three phase transformer over a bank of three single phase transformer.
- l) Give any two advantages of star-star connection in 3-  $\phi$  transformers.

2. Attempt any FOUR of the following:

16

- a) Distinguish between lap and wave winding. (Any four points)
- b) Determine the flux per pole of a six pole generator required to generate 240V at 500rpm. The armature winding has 1080 conductors and are lap connected.
- c) Draw the circuit diagram of
  - (i) DC series motor
  - (ii) DC long shuntCompound motor. Also write down the related equation.
- d) What is Back emf in DC Motor? Explain its significance.
- e) Draw and explain the following characteristics in DC Shunt motor:
  - (i) Torque vs Armature current.
  - (ii) Speed vs Torque.
- f) A 500 V DC shunt motor takes a current of 5 Amp on no load. The resistances of the armature and field circuits are 0.5  $\Omega$  and 250  $\Omega$ . Calculate the efficiency when the motor takes a current of 100 Amp.

**3. Attempt any FOUR of the following:****16**

- a) With the help of neat diagrams, explain the following methods of speed control in DC series motor:
  - (i) Field diverter method
  - (ii) Armature diverter method.
- b) Give the classification of transformer based on:
  - (i) Construction
  - (ii) Voltage Level
  - (iii) Number of phases
  - (iv) Applications
- c) Compare core type and shell type transformer on any four parameters.
- d) Derive the emf equation of a transformer.
- e) Draw the connection diagram of Delta-star connection of 3- $\phi$  Transformer and give any two advantages and disadvantages of this connection.
- f) A 3300/230V, 50Hz single phase transformer is to be operated at a maximum flux density of  $1.2 \text{ Wb/m}^2$  in the core. The effective cross sectional area of the transformer is  $150 \text{ cm}^2$ . Calculate suitable values of primary and secondary turns.

**4. Attempt any FOUR of the following:****16**

- a) A 1- $\phi$  Transformer with a ratio of 440/110V takes a no load current of 5A at 0.2 pf lagging. If the secondary supplies a current of 120 Amp at a pf of 0.8 lagging, estimate the current taken by the primary.
- b) A 50 KVA, 4400/220 V transformer has  $R_1 = 3.45 \Omega$ ,  $R_2 = 0.009 \Omega$ . The value of reactances are  $X_1 = 5.2 \Omega$  and  $X_2 = 0.015 \Omega$  Calculate for the transformer:
  - (i) equivalent resistance and reactance as referred to HV side.
  - (ii) equivalent resistance and reactance as referred to LV side.

- c) Efficiency of 400KVA, 1- $\phi$  Transformer is 98.77% when delivering full load at 0.8 pf and it is 99.13% at half load unity pf. Calculate:
- Iron Loss
  - Full load copper loss
- d) Two, 1-phase transformers with equal turns have impedance of  $(0.5 + j3)\Omega$  and  $(0.6 + j10)\Omega$  with respect to the secondary. If they are operated in parallel, determine how they will share a total load of 100 kW at a pf of 0.8 lagging?
- e) Draw a neat experimental set up to conduct OC Test on a single phase transformer. Also give reason why it is preferable to conduct OC Test on LV side?
- f) Describe the different losses in a transformer. And what measures should be taken to minimize them?

**5. Attempt any FOUR of the following:**

**16**

- a) Give any two advantages of parallel operation and any two conditions to be satisfied for parallel operation of 1- $\phi$  transformers.
- b) A 1 phase 50 kVA, 2400/120V, 50Hz transformer gave following test results:-  
 OC Test (Instruments on LV side): 120V, 9.85A, 396W  
 SC Test (Instruments on HV side): 92V, 20.8A, 810W  
 Calculate:
- The equivalent circuit constants
  - Efficiency at Rated KVA and 0.8 pf lagging.
- c) Find the all day efficiency of 500 kVA distribution transformer whose copper and iron losses at full load are 4.5 kW and 3 kW. It is loaded as under per day:

No. of hours	6	6	8	4
Load in kW	450	300	150	0
Power factor	0.9	0.75	1	—

- d) Draw the connection diagram and phasor diagram of star-delta connection used for 3 phase transformer connection.

- e) Compare Power and Distribution Transformer on the following parameters:
- (i) Typical voltages
  - (ii) Power Ratings
  - (iii) Size
  - (iv) Load
  - (v) Insulation level
  - (vi) Installation
  - (vii) Maximum efficiency
  - (viii) Type of efficiency
- f) With the help of neat diagram, explain the procedure of phasing out test on 3 phase transformer.

**6. Attempt any FOUR of the following:**

**16**

- a) Describe the construction and operation of three phase autotransformer with the help of neat diagram.
  - b) Illustrate the saving in copper by using 1- $\phi$  auto transformer instead of two winding transformer of the same rating by deriving proper expressions.
  - c) With the help of neat diagram, explain the construction of current transformer.
  - d) Draw schematic diagram of a welding transformer showing constructional features of a welding transformer. Also explain its working.
  - e) What is an isolation transformer? State any two applications of isolation transformer.
  - f) Draw a neat connection diagram of potential transformer. Also explain the two types of error that are likely to occur in the P.T.
-