



11819

17659

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) *All questions are compulsory.*
 - (2) *Answer each next main question on a new page.*
 - (3) *Illustrate your answers with neat sketches wherever necessary.*
 - (4) *Figures to the right indicate full marks.*
 - (5) *Assume suitable data, if necessary.*

Marks

1. A) Attempt **any three** : **(3×4=12)**
- 1) Compare Asynchronous sequential and synchronous sequential circuits.
 - 2) Explain estimation of channel capacitance of CMOS.
 - 3) Draw CMOS two input NOR gate and write it's truth table.
 - 4) State any 4 features of VHDL.
- B) Attempt **any one** : **(1×6=6)**
- 1) Compare FPGA and CPLD (any six pts.)
 - 2) State any one process for wafer fabrication with diagram.
2. Attempt **any four** : **(4×4=16)**
- 1) Explain fabrication using N-well process.
 - 2) Design $Y = \overline{AB} \cdot \overline{CD}$ using CMOS logic.
 - 3) What do you mean by simulation ? Why it is necessary ?
 - 4) Compare Mealy M/C with Moore M/C.
 - 5) Write VHDL code for half adder.
3. Attempt **any four** : **(4×4=16)**
- 1) Write the syntax of entity and architecture used in VHDL and explain it.
 - 2) Draw 2 : 4 decoder and write VHDL code for it.
 - 3) Describe Twin-tube process with diagram.
 - 4) What do you meant by sensitivity list and zero modeling ?
 - 5) Compare signals and variables in VHDL.

P.T.O.

**4. A) Attempt any three :****(3×4=12)**

- 1) Define the following terms :
 - i) Noise margin
 - ii) Power fanout
 - iii) Skew
 - iv) Meta stability
- 2) Explain event scheduling with suitable example.
- 3) What is test bench ? Write its applications.
- 4) List different concurrent statements and give the example of any two.

B) Attempt any one :**(1×6=6)**

- 1) Draw architecture of XC9500 CPLD.
- 2) Design a sequence detector to detect the sequence 110. Use D F/F to design the circuit.

5. Attempt any four :**(4×4=16)**

- 1) Draw the HDL design flow for synthesis.
- 2) State the function of each step elements of VHDL.
- 3) Draw CMOS inverter characteristic and explain it.
- 4) Write VHDL code for 4 : 1 MUX.
- 5) List the types of FSM. Draw labelled diagram of each.

6. Attempt any four :**(4×4=16)**

- 1) Explain basic architecture of Spaston-3 FPGA series.
 - 2) Write VHDL code for 3-bit down counter.
 - 3) Draw design flow of ASIC and explain it.
 - 4) Explain the shift and logical operations.
 - 5) State different modeling styles used in VHDL and write VHDL code for 1 : 4 DEMUX using any one style.
-